

超大型積體電路設計

VLSI Design

Homework V



國立清華大學

系所:電子所碩二

中文姓名:李聖謙

學號:111063517

授課老師:謝志成

Contents

1. Please design a 5-bit binary synchronous up counter with clock frequency CLK = 400MHz, VDD = 1.8V (default) , VSS = 0V. You can use any architecture to complete the design. Try to minimize the power consumption of the counter. You can adjust the value of VDD for minimizing the power meanwhile the counter works correctly, and the maximum glitch should be less than 80ps.....	2
(a) Please describe how you design the counter and how to reduce the glitch and power consumption of counter. (40%)	2
(b) Please list the glitch in each number (0 ~ 31) and find the maximum glitch. (20%)	2
(c) Please measure the power of the counter. (5%)	2
2. Please design a 5-bit pseudo-random-bit-sequence (PRBS) generator with Linear Feedback Shift Register (LFSR) with clock frequency CLK = 400MHz, VDD = 1.8V (default), VSS = 0V. Try to minimize the power consumption of the PRBS generator.	15
(a) Please describe how you design the PRBS generator and show the pseudo-randomsequence result to prove your design. (20%)	15
(b) Please measure the power of the PRBS generator. (5%)	17

1. Please design a 5-bit binary synchronous up counter with clock frequency CLK = 400MHz, VDD = 1.8V (default) , VSS = 0V. You can use any architecture to complete the design. Try to minimize the power consumption of the counter. You can adjust the value of VDD for minimizing the power meanwhile the counter works correctly, and the maximum glitch should be less than 80ps.
- (a) Please describe how you design the counter and how to reduce the glitch and power consumption of counter. (40%)
- (b) Please list the glitch in each number (0 ~ 31) and find the maximum glitch. (20%)
- (c) Please measure the power of the counter. (5%)

本題沿用 hw4 的 DFF 與 unit inverter 規格。

Size	Inverter	2-inputs NAND
PMOS	1.8u/0.18u, m = 1	1.04u/0.18u, m = 1
NMOS	0.6u/0.18u, m = 1	1.2u/0.18u, m = 1

Table 1 Siz

Schematic

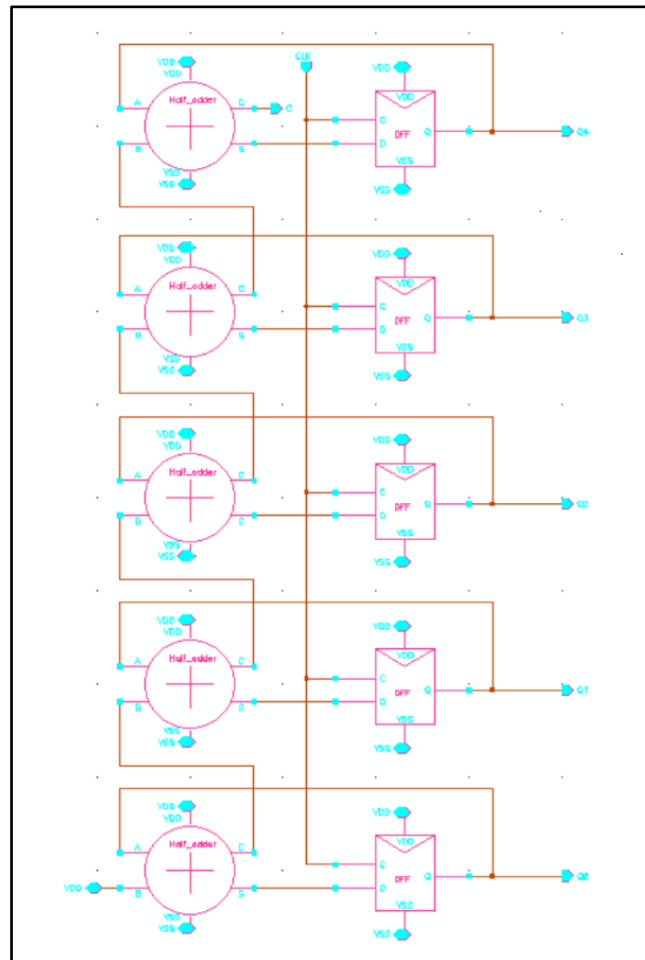


Figure 1 5-bit binary synchronous up counter schematic

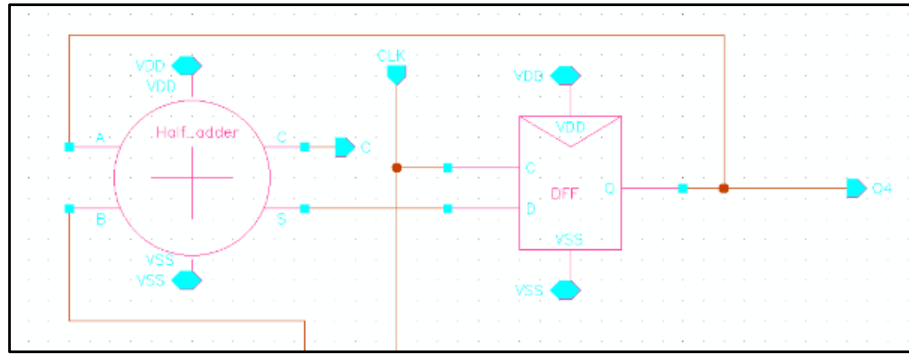


Figure 2 Each bit binary synchronous up counter schematic

 


Figure 3 DFF symbol

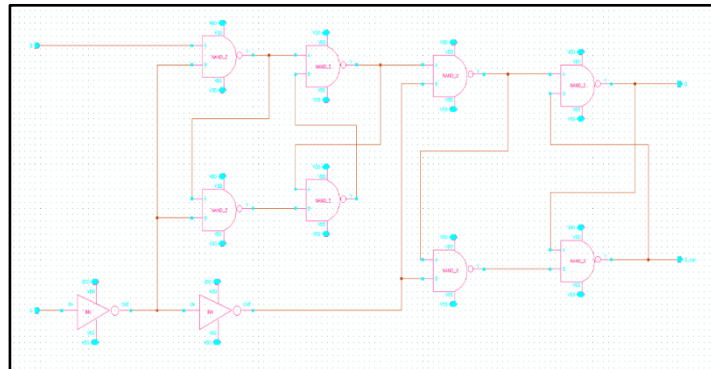


Figure 4 DFF schematic

 


Figure 5 Half_adder symbol

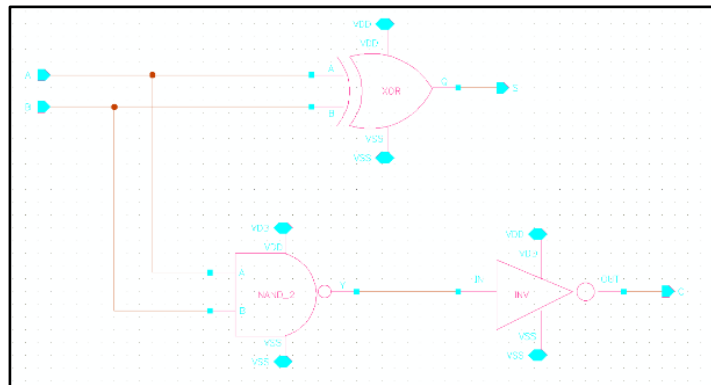


Figure 6 Half_adder schematic

 


Figure 7 XOR symbol

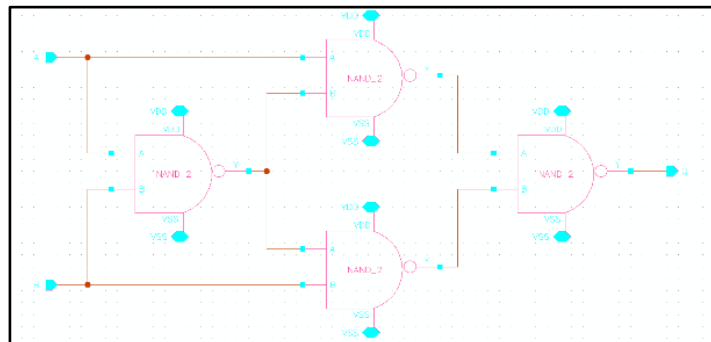


Figure 8 XOR schematic

 


Figure 9 Unit inverter symbol

 


Figure 10 Unit inverter schematic

 


Figure 11 2-inputs NAND gate symbol

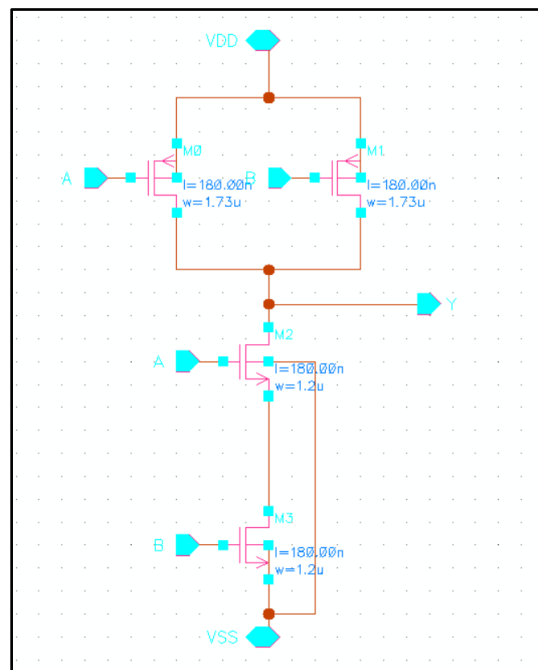


Figure 12 2-inputs NAND gate schematic

設計想法：

與講義上的 synchronous counter 相同，由 half adder 和 flip flop 組成，half adder 會產生 sum 和 carry，分別存進 flip flop 和下一級 half adder 輸入，來實現 counter 功能。其中大部分的底層的邏輯閘選擇使用 NAND 和 inverter 組合，原因是 NAND 相較於 NOR 可以使用較小的 MOS 尺寸，進而達到題目要求的降低功耗要求。

Glitch 原理:

Glitch 發生的原因是因為在計數時，同時有兩個 bit 的改變，因電壓在轉態過程所造成多餘且錯誤的值，例如在 1 轉換為 2 的過程，5bits 的 counter 會從 00001 變 00010，故中間會有一小段時間為第 4 個 bit 上升，第 5 個 bit 下降，因實際上 0 和 1 的變化是由電壓升降來實現，所以輸出會有一個瞬間會變為 00011，下方以 15~16 為例:

 


Figure 13



在 15~16 是由 01111→10000，轉態中會有 4 個 glitch 值，故分別為 31、30、28、24，在波型上可知當 glitch value = 24 時有最長的 glitch time，故在後面的表格我將最長的 glitch time 標示成紅色，表示完整的 glitch time。

造成這個現象的原因我認為和 data 的 rising 和 falling 有關，在 HW4 時討論了在 DFF 中 rising 和 falling 的差別，rsising 時間都比 falling 來的短，所以 glitch value 會先被拉大(所有 bit 都是 on 的狀態)。接著推測因 counter 的電路設計故 falling 會從低的 bit 依序 off。



Figure 14



Figure16 為 31~0(11111→00000)的波型，推測因為都是 falling 的轉態，故相較前面的 glitch time 減少許多。

Result

 


Figure 15 5-bit binary synchronous up counter waveform

***** transient analysis tnom= 25.000 temp= 25.000 *****					
glitch_1_2_->3=	28.0288p	targ= 7.7668n	trig= 7.7388n		
glitch_3_4_->7=	28.0354p	targ= 12.7668n	trig= 12.7388n		
glitch_3_4_->6=	28.1919p	targ= 12.7670n	trig= 12.7388n		
glitch_5_6_->7=	28.0256p	targ= 17.7667n	trig= 17.7386n		
glitch7_8_->15=	28.0270p	targ= 22.7659n	trig= 22.7379n		
glitch7_8_->14=	28.1935p	targ= 22.7661n	trig= 22.7379n		
glitch7_8_->12=	28.3389p	targ= 22.7662n	trig= 22.7379n		
glitch9_10_->11=	27.9716p	targ= 27.7658n	trig= 27.7379n		
glitch11_12_->15=	28.0180p	targ= 32.7666n	trig= 32.7386n		
glitch11_12_->14=	28.1809p	targ= 32.7668n	trig= 32.7386n		
glitch13_14_->15=	27.9693p	targ= 37.7667n	trig= 37.7387n		
glitch15_16_->31=	27.9874p	targ= 42.7659n	trig= 42.7379n		
glitch15_16_->30=	28.1519p	targ= 42.7660n	trig= 42.7379n		
glitch15_16_->28=	28.3010p	targ= 42.7662n	trig= 42.7379n		
glitch15_16_->24=	28.4369p	targ= 42.7663n	trig= 42.7379n		
glitch17_18_->19=	27.9971p	targ= 47.7659n	trig= 47.7379n		
glitch19_20_->23=	27.9983p	targ= 52.7659n	trig= 52.7379n		
glitch19_20_->22=	28.1588p	targ= 52.7660n	trig= 52.7379n		
glitch21_22_->23=	28.0264p	targ= 57.7659n	trig= 57.7379n		
glitch23_24_->31=	27.9915p	targ= 62.7659n	trig= 62.7379n		
glitch23_24_->30=	28.1544p	targ= 62.7660n	trig= 62.7379n		
glitch23_24_->28=	28.2959p	targ= 62.7662n	trig= 62.7379n		
glitch25_26_->27=	27.9933p	targ= 67.7658n	trig= 67.7378n		
glitch27_28_->31=	28.0343p	targ= 72.7660n	trig= 72.7379n		
glitch27_28_->30=	28.1938p	targ= 72.7661n	trig= 72.7379n		
glitch29_30_->31=	28.0467p	targ= 77.7667n	trig= 77.7387n		
glitch31_0_->30=	162.5383f	targ= 82.7669n	trig= 82.7667n		
glitch31_0_->28=	147.0692f	targ= 82.7671n	trig= 82.7669n		
glitch31_0_->24=	139.3144f	targ= 82.7672n	trig= 82.7671n		
glitch31_0_->16=	133.4034f	targ= 82.7673n	trig= 82.7672n		
pvdd=-744.5465u		from= 5.0000n	to= 85.0000n		

Figure 16 Glitch & power consumption

Power consumption = 744.5465μW

上圖為每一個 glitch 的時間長度與 glitch 的值，由波形可以看出 glitch 僅發生在奇數變偶數的時刻，故只標出有 glitch 的時間，下方用表格表示

Number to number	Glitch value	Glitch time	
1~2	3	28.2088ps	
3~4	7	28.0354ps	
	6	28.1919ps	
5~6	7	28.0256ps	
7~8	15	28.0270ps	
	14	28.1935ps	
	12	28.3389ps	
9~10	11	27.9716ps	
11~12	15	28.0180ps	
	14	28.1809ps	
13~14	15	27.9693ps	
15~16	31	27.9874ps	
	30	28.1519ps	
	28	28.3010ps	
	24	28.4369ps	
17~18	19	27.9971ps	
19~20	23	27.9983ps	
	22	28.1588ps	
21~22	23	28.0264ps	
23~24	31	27.9915ps	
	30	28.1544ps	
	28	28.2959ps	
25~26	27	27.9933ps	
27~28	31	28.0343ps	
	30	28.1938ps	
29~30	31	28.0467ps	
31~0	30	162.5383fs	582.3253fs
	28	147.0692fs	
	24	139.3144fs	
	16	133.4034fs	

Table 2 Glitch(紅字代表該數字轉換的總 glitch time)

Maximum glitch = 28.4369ps

Glitch and power consumption reduce method:

I. Reduce the VDD to 1.1V

 


Figure 17 5-bit binary synchronous up counter waveform

***** transient analysis tnom= 25.000 temp= 25.000 *****					
glitch_1_2_->3=	78.2977p	targ=	8.0300n	trig=	7.9517n
glitch_3_4_->7=	78.4741p	targ=	13.0305n	trig=	12.9520n
glitch_3_4_->6=	79.1479p	targ=	13.0312n	trig=	12.9520n
glitch_5_6_->7=	78.4326p	targ=	18.0300n	trig=	17.9516n
glitch7_8_->15=	78.3765p	targ=	23.0304n	trig=	22.9520n
glitch7_8_->14=	79.0134p	targ=	23.0310n	trig=	22.9520n
glitch7_8_->12=	79.5790p	targ=	23.0316n	trig=	22.9520n
glitch9_10_->11=	78.1942p	targ=	28.0295n	trig=	27.9513n
glitch11_12_->15=	78.2415p	targ=	33.0303n	trig=	32.9521n
glitch11_12_->14=	78.9021p	targ=	33.0310n	trig=	32.9521n
glitch13_14_->15=	78.1507p	targ=	38.0294n	trig=	37.9513n
glitch15_16_->31=	78.5946p	targ=	43.0297n	trig=	42.9511n
glitch15_16_->30=	79.2462p	targ=	43.0304n	trig=	42.9511n
glitch15_16_->28=	79.8312p	targ=	43.0310n	trig=	42.9511n
glitch15_16_->24=	80.4022p	targ=	43.0315n	trig=	42.9511n
glitch17_18_->19=	78.1306p	targ=	48.0294n	trig=	47.9513n
glitch19_20_->23=	78.4186p	targ=	53.0305n	trig=	52.9520n
glitch19_20_->22=	79.0821p	targ=	53.0311n	trig=	52.9520n
glitch21_22_->23=	78.5621p	targ=	58.0304n	trig=	57.9519n
glitch23_24_->31=	78.2579p	targ=	63.0303n	trig=	62.9520n
glitch23_24_->30=	78.9578p	targ=	63.0310n	trig=	62.9520n
glitch23_24_->28=	79.5821p	targ=	63.0316n	trig=	62.9520n
glitch25_26_->27=	78.2572p	targ=	68.0296n	trig=	67.9513n
glitch27_28_->31=	78.5259p	targ=	73.0306n	trig=	72.9521n
glitch27_28_->30=	79.1723p	targ=	73.0313n	trig=	72.9521n
glitch29_30_->31=	78.4259p	targ=	78.0303n	trig=	77.9519n
glitch31_0_->30=	703.3738f	targ=	83.0310n	trig=	83.0303n
glitch31_0_->28=	634.0452f	targ=	83.0316n	trig=	83.0310n
glitch31_0_->24=	630.6190f	targ=	83.0323n	trig=	83.0316n
glitch31_0_->16=	749.5133f	targ=	83.0330n	trig=	83.0323n
pvdd=-259.4326u from= 5.0000n to= 85.0000n					

Figure 18 Glitch & power consumption

Power consumption = 259.4326μW

選擇 VDD = 1.1V 的原因是因為可以維持電路正常運作，若 VDD=1V 電路將會出錯。

Number to number	Glitch value	Glitch time	
1~2	3	78.2977ps	
3~4	7	78.4741ps	
	6	79.1479ps	
5~6	7	78.4326ps	
7~8	15	78.3765ps	
	14	79.0134ps	
	12	79.5790ps	
9~10	11	78.1942ps	
11~12	15	78.2415ps	
	14	78.9021ps	
13~14	15	78.1507ps	
15~16	31	78.5946ps	
	30	79.2462ps	
	28	79.8312ps	
	24	80.4022ps	
17~18	19	78.1306ps	
19~20	23	78.4186ps	
	22	79.0821ps	
21~22	23	78.5621ps	
23~24	31	78.2579ps	
	30	78.9578ps	
	28	79.5821ps	
25~26	27	78.2572ps	
27~28	31	78.5259ps	
	30	79.1723ps	
29~30	31	78.4259ps	
31~0	30	703.3738fs	2.718ps
	28	634.0452fs	
	24	630.6190fs	
	16	749.5133fs	

Table 3 Glitch(紅字代表該數字轉換的總 glitch time)

Maximum glitch = 80.4022ps

降低 VDD 後可以發現 power consumption 明顯下降(744μW→259μW)，但 glitch 卻也上升多(28ps→78ps)，故有可能因此造成電路不正常運作。

II. Reduce the unit inverter size

Size	Inverter	2-inputs NAND
PMOS	0.9u/0.18u, m = 1	0.52u/0.18u, m = 1
NMOS	0.3u/0.18u, m = 1	0.6u/0.18u, m = 1

Table 4 Resize

 


Figure 19 5-bit binary synchronous up counter waveform

***** transient analysis tnom= 25.000 temp= 25.000 *****			
glitch_1_2_->3=	28.1748p	targ= 7.7616n	trig= 7.7334n
glitch_3_4_->7=	28.1781p	targ= 12.7616n	trig= 12.7334n
glitch_3_4_->6=	28.3355p	targ= 12.7618n	trig= 12.7334n
glitch_5_6_->7=	28.2117p	targ= 17.7616n	trig= 17.7333n
glitch7_8_->15=	28.2012p	targ= 22.7617n	trig= 22.7335n
glitch7_8_->14=	28.3655p	targ= 22.7618n	trig= 22.7335n
glitch7_8_->12=	28.5083p	targ= 22.7620n	trig= 22.7335n
glitch9_10_->11=	28.2135p	targ= 27.7616n	trig= 27.7333n
glitch11_12_->15=	28.2120p	targ= 32.7616n	trig= 32.7334n
glitch11_12_->14=	28.3702p	targ= 32.7618n	trig= 32.7334n
glitch13_14_->15=	28.1764p	targ= 37.7616n	trig= 37.7334n
glitch15_16_->31=	28.1756p	targ= 42.7616n	trig= 42.7334n
glitch15_16_->30=	28.3370p	targ= 42.7618n	trig= 42.7334n
glitch15_16_->28=	28.4841p	targ= 42.7619n	trig= 42.7334n
glitch15_16_->24=	28.6180p	targ= 42.7621n	trig= 42.7334n
glitch17_18_->19=	28.1999p	targ= 47.7617n	trig= 47.7335n
glitch19_20_->23=	28.2100p	targ= 52.7626n	trig= 52.7344n
glitch19_20_->22=	28.3681p	targ= 52.7628n	trig= 52.7344n
glitch21_22_->23=	28.1499p	targ= 57.7625n	trig= 57.7343n
glitch23_24_->31=	28.1786p	targ= 62.7616n	trig= 62.7334n
glitch23_24_->30=	28.3408p	targ= 62.7618n	trig= 62.7334n
glitch23_24_->28=	28.4826p	targ= 62.7619n	trig= 62.7334n
glitch25_26_->27=	28.2120p	targ= 67.7626n	trig= 67.7344n
glitch27_28_->31=	28.1612p	targ= 72.7616n	trig= 72.7335n
glitch27_28_->30=	28.3210p	targ= 72.7618n	trig= 72.7335n
glitch29_30_->31=	28.1827p	targ= 77.7626n	trig= 77.7344n
glitch31_0_->30=	165.0519f	targ= 82.7618n	trig= 82.7617n
glitch31_0_->28=	148.1577f	targ= 82.7620n	trig= 82.7618n
glitch31_0_->24=	139.5179f	targ= 82.7621n	trig= 82.7620n
glitch31_0_->16=	132.9963f	targ= 82.7623n	trig= 82.7621n
pvdd=-387.3136u from= 5.0000n to= 85.0000n			

Figure 20 Glitch & power consumption

Power consumption = 387.3136μW

Number to number	Glitch value	Glitch time	
1~2	3	28.1748ps	
3~4	7	28.1781ps	
	6	28.3355ps	
5~6	7	28.2117ps	
7~8	15	28.2012ps	
	14	28.3665ps	
	12	28.5083ps	
9~10	11	28.2135ps	
11~12	15	28.2120ps	
	14	28.3702ps	
13~14	15	28.1764ps	
15~16	31	28.1756ps	
	30	28.3370ps	
	28	28.4841ps	
	24	28.6180ps	
17~18	19	28.1999ps	
19~20	23	28.2100ps	
	22	28.3681ps	
21~22	23	28.1499ps	
23~24	31	28.1786ps	
	30	28.3408ps	
	28	28.4826ps	
25~26	27	28.2120ps	
27~28	31	28.1612ps	
	30	28.3210ps	
29~30	31	28.1827ps	
31~0	30	165.0510fs	585.7229fs
	28	148.1577fs	
	24	139.5179fs	
	16	132.9963fs	

Table 5 Glitch(紅字代表該數字轉換的總 glitch time)

Maximum glitch = 28.6180p

降低 unit inverter size 後可以發現 power consumption 也有下降，雖然沒有調低 VDD 來的顯著(744μW→387μW)，但在 glitch 卻和原本 size 時的時間差不多，沒有因此上升。

III. Reduce VDD & unit inverter size

在已知調低 unit inverter size 會降低 power 並且 glitch 不太放大的情況下，加上調低 VDD 可以大幅下降 power consumption，故結合兩者的優點，理論上，較小的 unit inverter size 可以在更低的 VDD 下正常運作電路如下。

 


Figure 21 5-bit binary synchronous up counter waveform

***** transient analysis tnom= 25.000 temp= 25.000 *****					
glitch_1_2_->3=	75.1808p	targ= 8.0175n	trig= 7.9423n		
glitch_3_4_->7=	75.4132p	targ= 13.0172n	trig= 12.9418n		
glitch_3_4_->6=	76.0834p	targ= 13.0179n	trig= 12.9418n		
glitch_5_6_->7=	75.1924p	targ= 18.0173n	trig= 17.9421n		
glitch7_8_->15=	75.1010p	targ= 23.0173n	trig= 22.9422n		
glitch7_8_->14=	75.8006p	targ= 23.0180n	trig= 22.9422n		
glitch7_8_->12=	76.4258p	targ= 23.0186n	trig= 22.9422n		
glitch9_10_->11=	75.1151p	targ= 28.0173n	trig= 27.9422n		
glitch11_12_->15=	75.2598p	targ= 33.0174n	trig= 32.9421n		
glitch11_12_->14=	75.9397p	targ= 33.0181n	trig= 32.9421n		
glitch13_14_->15=	75.4027p	targ= 38.0175n	trig= 37.9421n		
glitch15_16_->31=	75.4941p	targ= 43.0177n	trig= 42.9422n		
glitch15_16_->30=	76.1558p	targ= 43.0184n	trig= 42.9422n		
glitch15_16_->28=	76.7543p	targ= 43.0190n	trig= 42.9422n		
glitch15_16_->24=	77.3213p	targ= 43.0195n	trig= 42.9422n		
glitch17_18_->19=	75.3476p	targ= 48.0174n	trig= 47.9421n		
glitch19_20_->23=	75.1106p	targ= 53.0174n	trig= 52.9423n		
glitch19_20_->22=	75.7781p	targ= 53.0180n	trig= 52.9423n		
glitch21_22_->23=	75.5536p	targ= 58.0179n	trig= 57.9423n		
glitch23_24_->31=	75.1078p	targ= 63.0169n	trig= 62.9418n		
glitch23_24_->30=	75.7310p	targ= 63.0175n	trig= 62.9418n		
glitch23_24_->28=	76.3301p	targ= 63.0181n	trig= 62.9418n		
glitch25_26_->27=	75.2596p	targ= 68.0173n	trig= 67.9421n		
glitch27_28_->31=	75.5290p	targ= 73.0178n	trig= 72.9422n		
glitch27_28_->30=	76.1776p	targ= 73.0184n	trig= 72.9422n		
glitch29_30_->31=	75.0625p	targ= 78.0173n	trig= 77.9422n		
glitch31_0_->30=	701.7234f	targ= 83.0179n	trig= 83.0172n		
glitch31_0_->28=	638.0213f	targ= 83.0186n	trig= 83.0179n		
glitch31_0_->24=	615.2443f	targ= 83.0192n	trig= 83.0186n		
glitch31_0_->16=	740.3555f	targ= 83.0199n	trig= 83.0192n		
pvdd=-134.6626u		from= 5.0000n	to= 85.0000n		

Figure 22 Glitch & power consumption

Power consumption = 134.6626μW

Number to number	Glitch value	Glitch time	
1~2	3	75.1808ps	
3~4	7	75.4132ps	
	6	76.0834ps	
5~6	7	75.1924ps	
7~8	15	75.1010ps	
	14	75.8006ps	
	12	76.4258ps	
9~10	11	75.1151ps	
11~12	15	75.2598ps	
	14	75.9397ps	
13~14	15	75.4027ps	
15~16	31	75.4941ps	
	30	76.1558ps	
	28	76.7543ps	
	24	77.3213ps	
17~18	19	75.3476ps	
19~20	23	75.1106ps	
	22	75.7781ps	
21~22	23	75.5536ps	
23~24	31	75.1078ps	
	30	75.7310ps	
	28	76.3301ps	
25~26	27	75.2596ps	
27~28	31	75.5290ps	
	30	76.1776ps	
29~30	31	75.0625ps	
31~0	30	701.7234fs	2.695ps
	28	638.0213fs	
	24	615.2443fs	
	16	740.3555fs	

Table 6 Glitch(紅字代表該數字轉換的總 glitch time)

Maximum glitch = 77.3213ps

從結果來看，降低 VDD 和 unit inverter size 是可以並行的，因為結合兩者優點，使 power consumption 可以降到最低，maximum glitch 也符合題目要求的 80ps。

IV. Compared

	Power consumption	Maximum glitch
Original	744.5465 μ W	28.4369ps
Reduce VDD	259.4326 μ W	80.4022ps
Reduce size	387.3136 μ W	28.6180ps
Reduce both	134.6626 μ W	77.3213ps

Table 7 Compared

綜合 3 種降低 power consumption 和 maximum glitch 的策略，可以發現調低 VDD 是最有效可以降低 power consumption 的，但電路的 glitch 也因此上升，影響電路功能，相比之下降低 mos size 可以在不付出更多代價的情況下，也可以降低 power consumption。兩者結合雖然 glitch 也上升，但 size 調小後再降低 VDD 的 glitch 也較會因此縮小一些，有更大的容錯空間。

2. Please design a 5-bit pseudo-random-bit-sequence (PRBS) generator with Linear Feedback Shift Register (LFSR) with clock frequency CLK = 400MHz, VDD = 1.8V (default), VSS = 0V. Try to minimize the power consumption of the PRBS generator.
- (a) Please describe how you design the PRBS generator and show the pseudo-randomsequence result to prove your design. (20%)

Linear shift feedback register(LFSR)原理:

在電路上實現 5-bits 的 LFSR 需要用 5 個 flip flop 和 1 個 XOR gate，可以透過更換 XOR 的 input 得到不同的偽隨機 bits stream，會稱為偽隨機是因為產生的亂數是可以計算的，但 LFSR 無法產生為零的 bits。

以 5-bits 為例，LFSR 可以產生最多 31 種(2^n-1)不同 bits 為一循環的 bits stream，除此之外也可以產生每一循環都更少 bits 的搭配，下方舉兩個例子比較差異。

Type1: XOR inputs Q [4] & Q [5]

 


Figure 23 5-bits LFSR circuit design & state diagram

由推導 state diagram 可知將 XOR inputs 接在 Q [4]和 Q [5]可以得到 21 個 bits 為一循環的 LFSR。

Type2: XOR inputs Q [3] & Q [5]

 


Figure 24 5-bits LFSR circuit design & state diagram

由推導 state diagram 可知將 XOR inputs 接在 Q [3]和 Q [5]可以得到 31 個 bits 為一循環的 LFSR。相比第一種設計，接在 Q[3]可以產生更多的偽隨機亂數，故本題採用第二種設計方法。

Schematic:

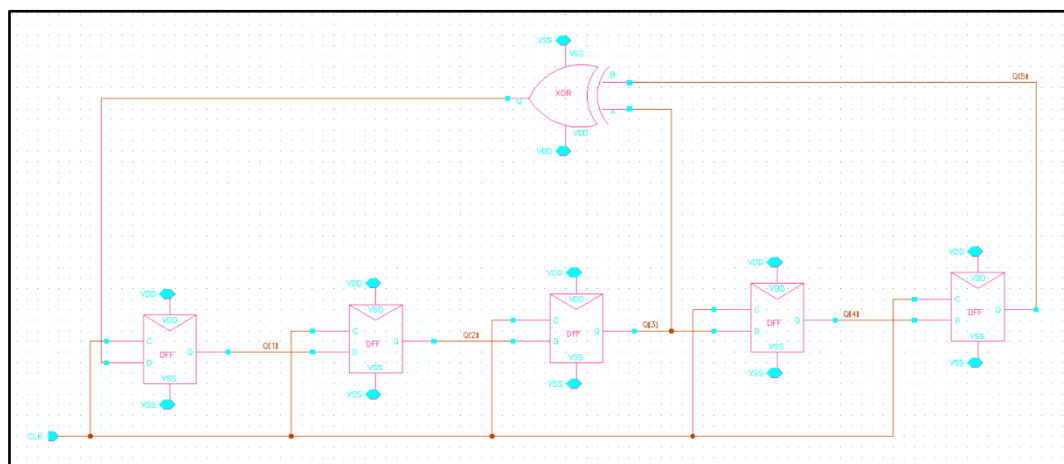


Figure 25

(b) Please measure the power of the PRBS generator. (5%)

此處採用與第一題相同的元件尺寸。

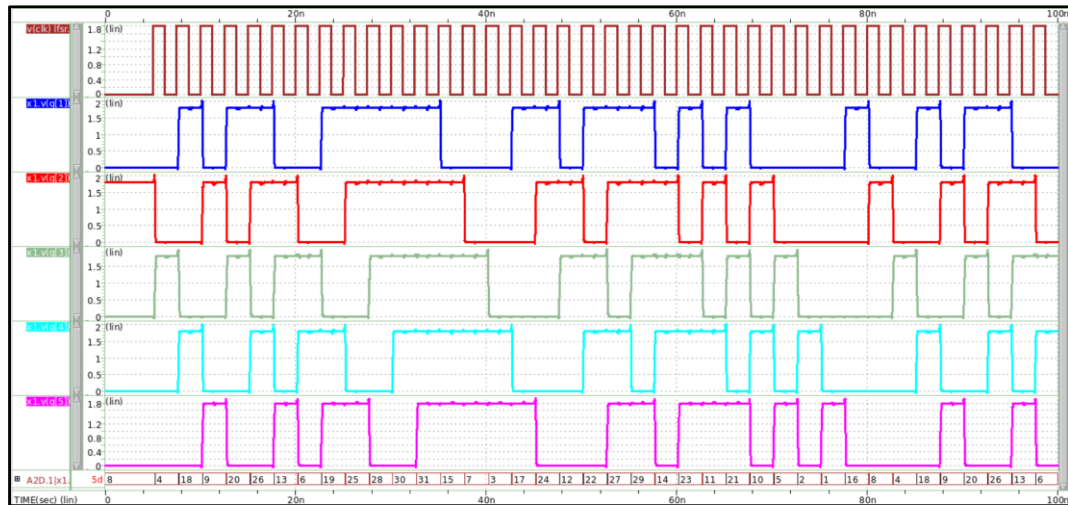


Figure 26 5-bit LFSR waveform

模擬與推導結果相符。

```
***** transient analysis tnom= 25.000 temp= 25.000 *****
pvdd=-585.6083u from= 5.0000n to= 82.5000n
```

Power consumption = 585.6083 μ W

Minimize power consumption method

I. Reduce the VDD to 1.1V

 


Figure 27 5-bit LFSR waveform

```
***** transient analysis tnom= 25.000 temp= 25.000 *****
pvdd=-200.8452u from= 5.0000n to= 82.5000n
```

Power consumption = 200.8452 μ W

II. Reduce the unit inverter size

Size	Inverter	2-inputs NAND
PMOS	0.9u/0.18u, m = 1	0.52u/0.18u, m = 1
NMOS	0.3u/0.18u, m = 1	0.6u/0.18u, m = 1

Table 8 Resize

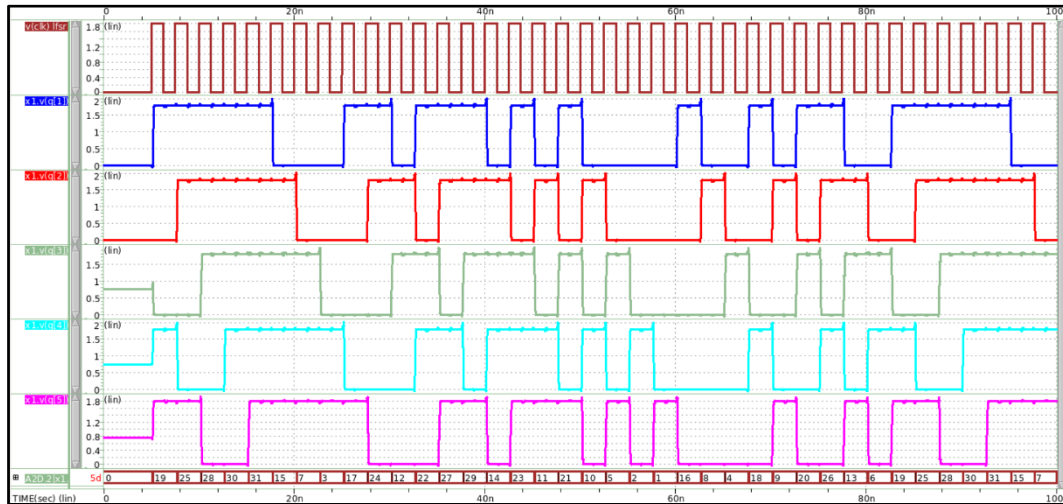


Figure 28 5-bit LFSR waveform

```
***** transient analysis tnom= 25.000 temp= 25.000 *****
pvdd=-306.0010u from= 5.0000n to= 82.5000n
```

Power consumption = 306.0010 μ W

III. Reduce VDD & unit inverter size

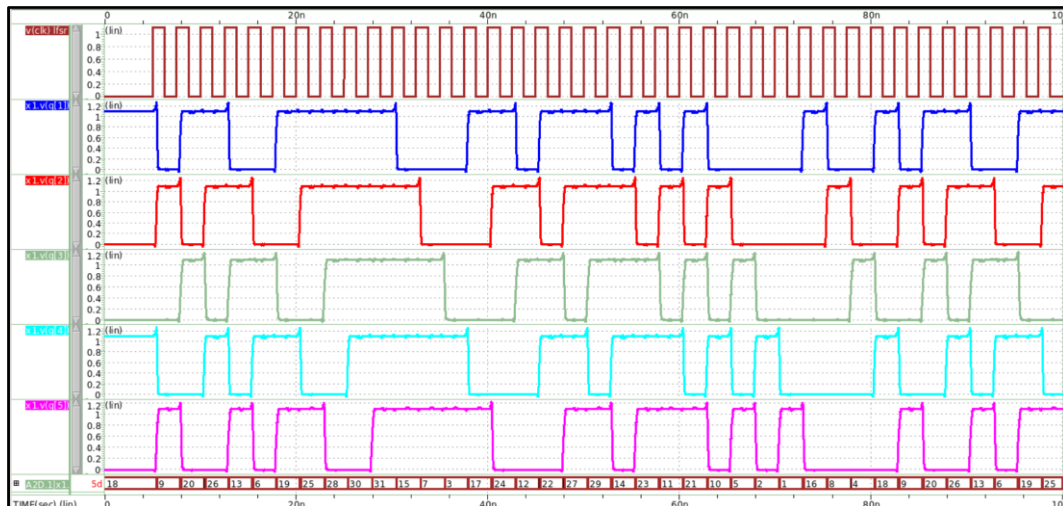


Figure 29 5-bit LFSR waveform

```
***** transient analysis tnom= 25.000 temp= 25.000 *****
pvdd=-104.6785u from= 5.0000n to= 82.5000n
```

Power consumption = 104.6785 μ W

IV. Compared

	Original	Reduce VDD	Reduce size	Reduce both
Power consumption	585.6083 μ W	200.8452 μ W	306.0010 μ W	104.6785 μ W

Table 9 Compared

綜合 3 種降低 power consumption 和 maximum glitch 的策略，可以發現趨勢與第一題相同，調低 VDD 是有效可以降低 power consumption 的，降低 size 效益最差，兩者皆降的表現最佳。