

2023 EE5250 VLSI Design Homework 5

Due date:2023/12/28

**Set temperature = 25 degrees for TT corner during simulation.*

**The following should be included in your report: (a) picture of the schematic, (b) picture of the waveform with cursor values, (c) your comment*

!!!This homework you just need to design under .18 um process!!!

1. Please design a **5-bit binary synchronous up counter** with clock frequency CLK = 400MHz, $V_{DD} = 1.8V$ (default) , $V_{SS} = 0V$. You can use any architecture to complete the design. **Try to minimize the power consumption of the counter.** You can adjust the value of V_{DD} for minimizing the power meanwhile the counter works correctly, and **the maximum glitch should be less than 80ps.**
 - (a) Please describe how you design the counter and how to reduce the glitch and power consumption of counter. (40%)
 - (b) Please list the glitch in each number (0 ~ 15) and find the maximum glitch. (20%)
 - (c) Please measure the power of the counter. (5%)

<Notice>

- The rising time and falling time of clock is **10ps**
- The time step in transient simulation should be $\leq 1ps$
- You can use the following code to measure the power, the time duration is a complete period.
`.measure tran PVDD AVG PAR('(V(Vdd)*I(Vdd))') from=___ to=___`
- You can use the '**A to D**' function in WaveView to convert the binary code to decimal value and check whether your function works.
 - i. select the waveform (B[0]~B[3]), click 'A to D'
 - ii. set the '**Center Logic Threshold**' to $0.5V_{DD}$, click 'OK' , there will be several waveforms at the bottom of the WaveView
 - iii. '**Group**' these waveforms and sort the signal order in Bus Configuration
 - iv. Right click the group waveforms '**Radix**', select '**Decimal**'.
- Remember that when you change the value of V_{DD} , you should change the '**Center Logic Threshold**' to $0.5V_{DD}$.

2. Please design a **5-bit pseudo-random-bit-sequence (PRBS) generator** with Linear Feedback Shift Register (LFSR) with clock frequency CLK = 400MHz, $V_{DD} = 1.8V$ (default), $V_{SS} = 0V$. **Try to minimize the power consumption of the PRBS generator.**
- (a) Please describe how you design the PRBS generator and show the pseudo-randomsequence result to prove your design. (20%)
- (b) Please measure the power of the PRBS generator. (5%)

<Notice>

- The rising time and falling time of clock is **10ps**
- The time step in transient simulation should be $\leq 1ps$
- You can use the following code to measure the power, the time duration is a complete period.

`.measure tran PVDD AVG PAR('(V(Vdd)*I(Vdd))') from=___ to=___`

** The following should be included in your report:*

(a) picture of schematic and clearly mark the name and unit of the x-axis and y-axis

(b) picture of waveform with cursor values

(c) your comment

By CCHsieh